

CME2203 Lab 3 Pre-lab

Name-Surname: Çağrı AYDIN

Student Number: 2021510010

Section: 2

Subject: Superposition Principle

(updated: 09/11/2022)

Pre-lab Procedure

- Each student must prepare the pre-lab and upload it **INDIVIDUALLY!**
- Upload as a **.PDF** file.
- Draw the schematic for the circuit in Figure 1 using LTSpice. Remember to put a **text label** in the following format:

2022-23 Fall

CME2203, LAB3

Name Surname, Student No

Section

1. Upload a **PDF** file including your circuit design and simulation results visible (see example in Figure 1)

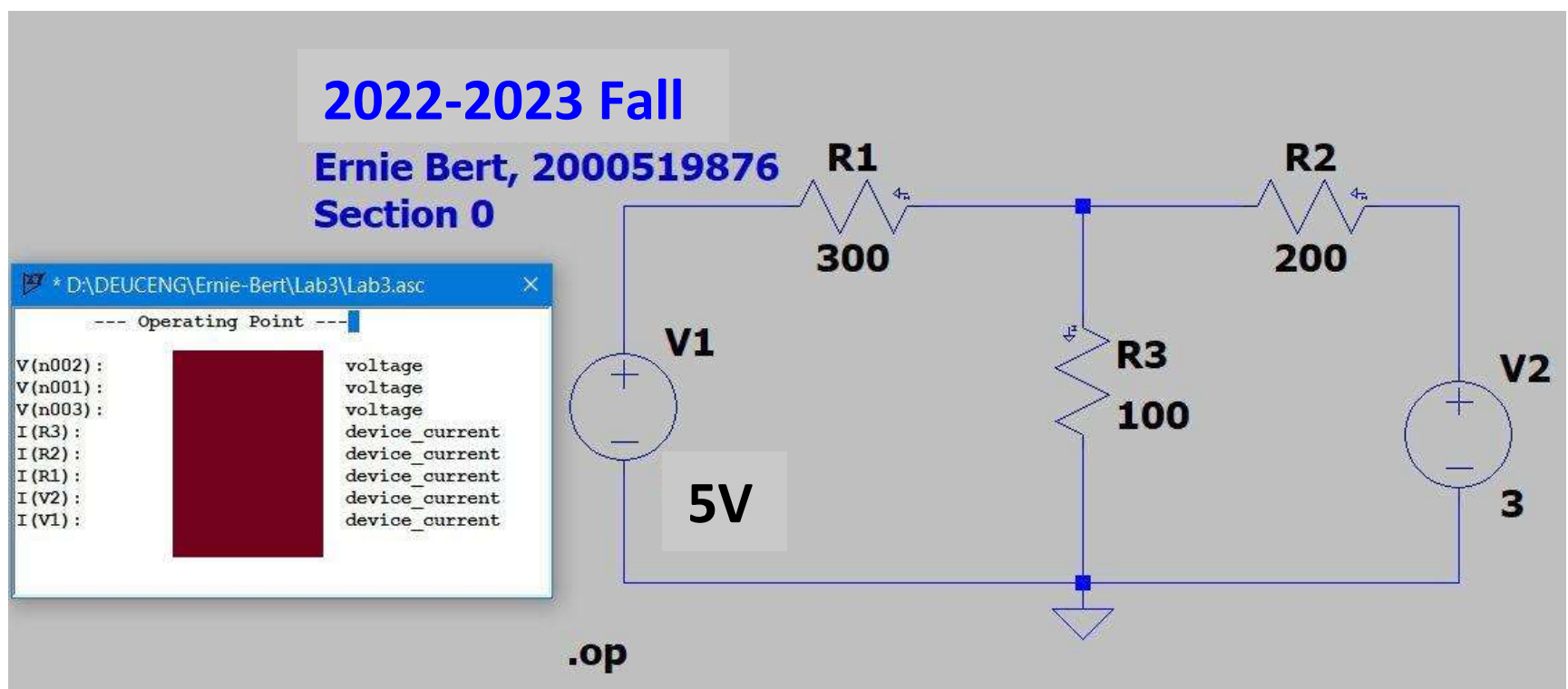


Figure 1 – Circuit Design in LtSpice

2. Note the simulation results and make the theoretical calculations using the superposition principle. You can use the tables given below. Compare the values and check if they are consistent.

Simulation Results from LTSpice

Circuit Element	I (mA)	V (V)
R1	$I(R1) = -0.0109091$	$n1-n2 = 3.27273$
R2	$I(R2) = 0.00636364$	$n2-n3 = -1.27273$
R3	$I(R3) = 0.0172727$	$n2 = 1.72727$


Fill the table below with your calculations. Add as many pages as necessary **to show your calculations to fill in the table below.**

		R1		R2		R3	
3V	5V	I1 (mA)	VR1 (V)	I2 (mA)	VR2 (V)	I3 (mA)	VR3 (V)
✓	-	2.72	0,816	10,9	2,18	8,17	0,816
-	✓	-13,63	4,089	-4,54	0,908	9,08	0,908
Total		-10,61	3,273	6,36	1,272	17,25	1,724

!!!No LATE submissions!!!Cheating will not be tolerated!!!

Good Luck...

Calculations Below:

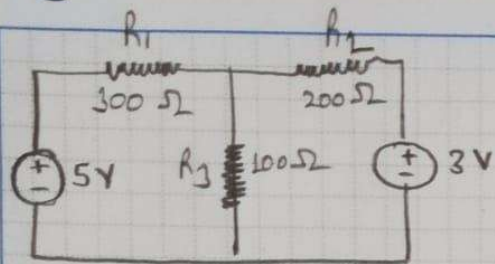

→ With out 3V supply

$$R_{eq} = 300 + \frac{200}{3} = 366,66 \Omega$$

R_2 and R_3 are parallel so $\Rightarrow \frac{1}{x} = \frac{1}{100} + \frac{1}{200} = \frac{3}{200} \quad x = \frac{200}{3}$

$$V = I \cdot R$$

$$5 = I \cdot 366,66$$

$$I = 0,01363 A$$

$$I_{R1} = 0,01363 A$$

$$V_{R1} = I_{R1} \cdot 300 = 4,089 V$$

$$2I_{R3} = I_{R2} \quad I_{R2} + I_{R3} = I_{R1}$$

$$I_{R2} = -0,00454 A$$

$$V_{R2} = I_{R2} \cdot 200 = 0,908 V$$

$$I_{R3} = 0,00908 A$$

$$V_{R3} = I_{R3} \cdot 100 = 0,908 V$$

→ With out 5V supply

$$R_{eq} = 200 + 75 = 275 \Omega$$

Now R_1 and R_2 are parallel so $\Rightarrow \frac{1}{x} = \frac{1}{300} + \frac{1}{100} = \frac{4}{300} \Rightarrow x = 75$

$$V = I \cdot R$$

$$3 = I \cdot 275$$

$$I = 0,0109$$

$$3I_{R1} = I_{R3} \quad \text{and} \quad I_{R1} + I_{R3} = I_{R2}$$

$$I_{R1} = 0,00272 A$$

$$V_{R1} = I_{R1} \cdot 300 = 0,816 V$$

$$I_{R2} = 0,0109 A$$

$$V_{R2} = I_{R2} \cdot 200 = 2,18 V$$

$$I_{R3} = 0,00817 A$$

$$V_{R3} = I_{R3} \cdot 100 = 0,816 V$$



T.C.
DOKUZ EYLÜL ÜNİVERSİTESİ
DOKUZ EYLÜL UNIVERSITY

ÖĞRENCİ KİMLİK KARTI

Adı ÇAĞRI

Soyadı AYDIN

Öğrenci No 2021510010

Birimi MÜHENDİSLİK FAK.

Unit

Bölümü/Prog. BİLGİSAYAR MÜH.


Department/Prog.

T.C. Kimlik No

ID Number



→ Calculating Total

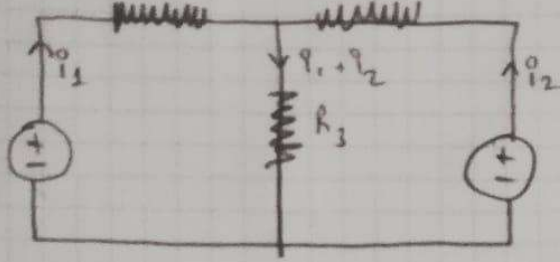

$$I_{R1} = i_1 + i_2 = 0,01363 A - 0,00292 A = \underline{0,01091 A}$$

$$I_{R2} = i_2 + i_1 = -0,00454 A + 0,01091 A = \underline{0,00636 A}$$

$$I_{R3} = i_1 + i_2 = 0,00908 A + 0,00819 A = \underline{0,01725 A}$$

$$V_{R1} = 0,01091 A \cdot 300 = \underline{3,273 V}$$

$$V_{R2} = 0,00636 A \cdot 200 = \underline{1,272 V}$$

$$V_{R3} = 0,01725 A \cdot 100 = \underline{1,724 V}$$



LTspice - [Pre-lab_3.asc]

File Edit Hierarchy View Simulate Tools Window Help

Pre-lab_3.asc

2022-23 FALL
CME2203, PreLAB3
Çağrı AYDIN, 2021510010
Section 2, Lab 4

.op

--- Operating Point ---

V(n002):	1.72727	voltage
V(n001):	5	voltage
V(n003):	3	voltage
I(R1):	-0.0109091	device_current
I(R2):	0.00636364	device_current
I(R3):	0.0172727	device_current
I(V1):	-0.0109091	device_current
I(V2):	-0.00636364	device_current

Ready

Ara

10:42
13.11.2023